

17 Using K-maps, find the minimal Boolean expressions of the following SOP and POS representations

(a) $f(w, x, y, z) = \sum (7, 13, 14, 15)$

(b) $f(w, x, y, z) = \sum (1, 3, 4, 6, 9, 11, 14, 15)$

(c) $f(w, x, y, z) = \prod (1, 4, 5, 6, 11, 12, 13, 14, 15)$

(d) $f(w, x, y, z) = \sum (1, 3, 4, 5, 7, 8, 9, 11, 15)$

(e) $f(w, x, y, z) = \prod (0, 4, 5, 7, 8, 9, 13, 15)$

Soln:

$f(w, x, y, z) = \sum (7, 13, 14, 15)$

$w \backslash xz$	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	0	1	1	1
10	0	0	0	0

Pair 1
 $w\bar{x}yz$
 $wxyz$

 wxz

Pair 2
 $\bar{w}xyz$
 $wxyz$

 xyz

Pair 3
 $wxyz$
 $wxy\bar{z}$

 wxy

$= wxz + xyz + wxy$

17 Using K-maps, find the minimal Boolean expressions of the following SOP and POS representations

(a) $f(w, x, y, z) = \sum (7, 13, 14, 15)$

(b) $f(w, x, y, z) = \sum (1, 3, 4, 6, 9, 11, 14, 15)$

(c) $f(w, x, y, z) = \prod (1, 4, 5, 6, 11, 12, 13, 14, 15)$

(d) $f(w, x, y, z) = \sum (1, 3, 4, 5, 7, 8, 9, 11, 15)$

(e) $f(w, x, y, z) = \prod (0, 4, 5, 7, 8, 9, 13, 15)$

Soln:

$f(w, x, y, z) = \sum (7, 13, 14, 15)$

		yz			
		00	01	11	10
wx	00				
	01			1	
	11		1	1	1
	10				

Pair 1	Pair 2	Pair 3
$w\bar{x}yz$	$\bar{w}xyz$	$wxyz$
$wxyz$	$wxyz$	$wxyz$
<hr/>	<hr/>	<hr/>
wxz	xyz	wxy

$= wxz + xyz + wxy$

17 Using K maps, find the minimal Boolean expressions of the following SOP and POS representations

(a) $f(w, x, y, z) = \sum (7, 13, 14, 15)$

(b) $f(w, x, y, z) = \sum (1, 3, 4, 6, 9, 11, 14, 15)$


(c) $f(w, x, y, z) = \prod (1, 4, 5, 6, 11, 12, 13, 14, 15)$

(d) $f(w, x, y, z) = \sum (1, 3, 4, 5, 7, 8, 9, 11, 15)$

(e) $f(w, x, y, z) = \prod (0, 4, 5, 7, 8, 9, 13, 15)$

Soln:

$f(w, x, y, z) = \sum (7, 13, 14, 15)$

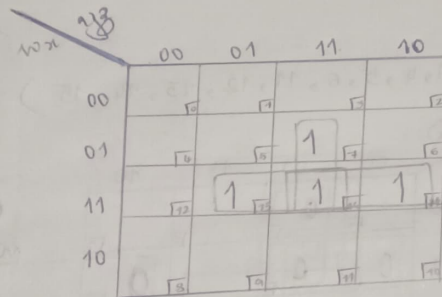

Pair 1

$$\frac{wx\bar{y}z}{wx\bar{y}z}$$

$$wxz$$

Pair 2

$$\frac{\bar{w}xyz}{\bar{w}xyz}$$

$$xyz$$

Pair 3

$$\frac{wx\bar{y}z}{wx\bar{y}z}$$

$$wx\bar{y}$$

$$= wxz + xyz + wx\bar{y}$$

17 Using K maps, find the minimal Boolean expressions of the following SOP and POS representations

(a) $f(w, x, y, z) = \sum (7, 13, 14, 15)$

(b) $f(w, x, y, z) = \sum (1, 3, 4, 6, 9, 11, 14, 15)$

(c) $f(w, x, y, z) = \prod (1, 4, 5, 6, 11, 12, 13, 14, 15)$

(d) $f(w, x, y, z) = \sum (1, 3, 4, 5, 7, 8, 9, 11, 15)$

(e) $f(w, x, y, z) = \prod (0, 4, 5, 7, 8, 9, 13, 15)$

Soln:

$f(w, x, y, z) = \sum (7, 13, 14, 15)$

$w \backslash x$		yz			
		00	01	11	10
	00				
	01			1	
	11		1	1	1
	10				

Pair 1

$$\frac{wx\bar{y}z + wxyz}{wxz}$$

Pair 2

$$\frac{\bar{w}xyz + wxyz}{xyz}$$

Pair 3

$$\frac{wx\bar{y}z + wxyz}{wxy}$$

$$= wxz + xyz + wxy$$

$$(b) f(w, x, y, z) = \sum (1, 3, 6, 9, 11, 14, 15)$$

Pair 1
 $wxyz$
 $wx\bar{y}$
 \underline{wxy}

Pair 2
 $\bar{w}xyz$
 $\bar{w}xy\bar{z}$
 $\underline{\bar{w}xz}$

$w \backslash xz$	00	01	11	10
00		1	1	
01	1			1
11			1	1
10		1	1	

Quad 1
 $\bar{w}xyz$
 $\bar{w}xy\bar{z}$
 $w\bar{x}yz$
 $w\bar{x}y\bar{z}$
 $\underline{\bar{x}z}$

Quad 1
 $\bar{w}xyz$
 $\bar{w}xy\bar{z}$
 $\bar{w}xyz$
 $\bar{w}xy\bar{z}$
 $\underline{\bar{w}z}$

Quad 2
 $\bar{w}xyz$
 $\bar{w}xy\bar{z}$
 $wxyz$
 $wxy\bar{z}$
 \underline{yz}

$$= wxy + \bar{w}xz + \bar{x}z$$

$$(c) f(w, x, y, z) = \prod (1, 4, 5, 6, 11, 12, 13, 14, 15)$$

Pair 1
 $w+x+y+z$
 $w+\bar{x}+y+\bar{z}$
 $\underline{w+y+\bar{z}}$

Pair 2
 $\bar{w}+\bar{x}+\bar{y}+\bar{z}$
 $\bar{w}+x+\bar{y}+\bar{z}$
 $\underline{\bar{w}+\bar{y}+\bar{z}}$

$w \backslash xz$	00	01	11	10
00		0		
01	0	0		0
11	0	0	0	0
10			0	

Quad 1
 $w+\bar{x}+y+z$
 $w+\bar{x}+y+\bar{z}$
 $\bar{w}+\bar{x}+y+z$
 $\bar{w}+\bar{x}+y+\bar{z}$
 $\underline{\bar{x}+\bar{y}}$

Quad 2
 $w+\bar{x}+y+z$
 $w+\bar{x}+y+\bar{z}$
 $w+\bar{x}+\bar{y}+z$
 $w+\bar{x}+\bar{y}+\bar{z}$
 $\underline{\bar{x}+z}$

Pair 1
 $w+x+y+z$
 $w+\bar{x}+y+z$
 $\underline{w+y+z}$

Pair 2
 $\bar{w}+\bar{x}+\bar{y}+\bar{z}$
 $\bar{w}+x+\bar{y}+\bar{z}$
 $\underline{\bar{w}+\bar{y}+\bar{z}}$

$$= (w+y+\bar{z}) \cdot (\bar{w}+\bar{y}+\bar{z}) \cdot (\bar{x}+y) \cdot (\bar{x}+z)$$

$$(e) f(w, x, y, z)$$

$$(d) f(w, x, y, z) = \sum (1, 3, 4, 5, 7, 8, 9, 11, 15)$$

Quad 1

$$\bar{w}\bar{x}\bar{y}z$$

$$\bar{w}\bar{x}yz$$

$$\bar{w}x\bar{y}z$$

$$\bar{w}xyz$$

$$\bar{w}z$$

Quad 2

$$\bar{w}\bar{x}yz$$

$$\bar{w}xyz$$

$$wx\bar{y}z$$

$$wx\bar{y}z$$

$$yz$$

$w \backslash yz$	00	01	11	10
00		1	1	
01	1	1	1	
11			1	
10	1	1	1	

Pair 1

$$\bar{w}\bar{x}\bar{y}z$$

$$\bar{w}\bar{x}yz$$

$$\bar{w}\bar{y}z$$

Pair 2

$$w\bar{x}\bar{y}z$$

$$w\bar{x}yz$$

$$w\bar{x}y$$

$$= \bar{w}z + yz + \bar{w}\bar{y}z + \bar{w}\bar{x}y$$

$$(e) f(w, x, y, z) = \prod (0, 4, 5, 7, 8, 9, 13, 15)$$

Pair 1

$$w+x+y+z$$

$$w+\bar{x}+y+z$$

$$w+y+z$$

Pair 2

$$\bar{w}+x+y+z$$

$$\bar{w}+x+y+\bar{z}$$

$$\bar{w}+x+z$$

$w \backslash yz$	00	01	11	10
00	0			
01	0	0	0	
11		0	0	
10	0	0		

Quad 1

$$w+\bar{x}+y+\bar{z}$$

$$\bar{w}+\bar{x}+y+\bar{z}$$

$$w+\bar{x}+\bar{y}+\bar{z}$$

$$\bar{w}+\bar{x}+\bar{y}+\bar{z}$$

$$\bar{x} + \bar{z}$$


$$= (w+y+z) \cdot (\bar{w}+x+z) \cdot$$

$$(\bar{x} + \bar{z})$$

2> Simplify the given Boolean expression using K-map and implement the simplified expression using NOR gates

$$Y = \prod M(1, 3, 5, 8, 10) \cdot dc(12, 13, 14, 15)$$

Soln:

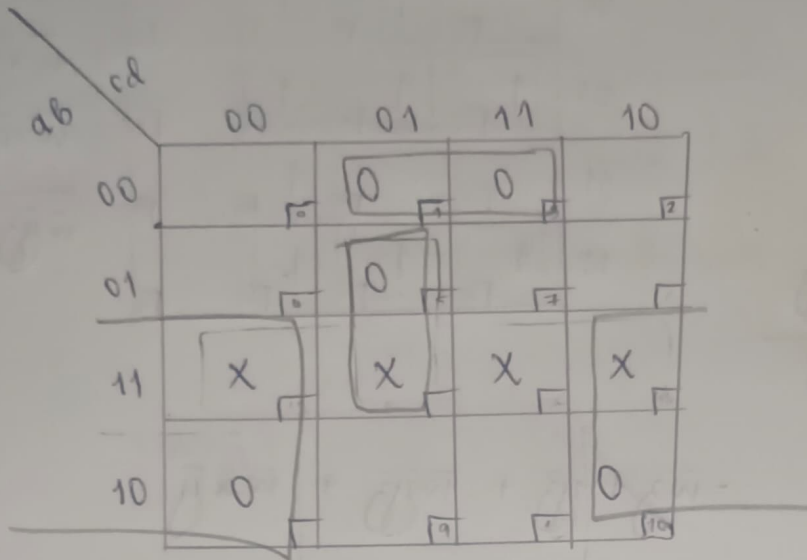

3>

the
a
in
th
of
in
l

→
→
→
→
→
→

3> A digital system is to be designed in which the months of the year is given as input in 4-bit form. The month January is represented as '0000', February as '0001' and so on. The output of the system is '0' corresponding to the input of the month the month containing 30 days or less otherwise it is '1'. Consider the excess number in the input beyond '1011' as don't care conditions. For this the system of 4 variables (A, B, C, D) find the

- Truth Table
- SOP expression $\leq m$
- POS expression TTM
- Simplified SOP expression using K-Map
- Basic gate implementation of simplified SOP expression
- Simplified POS expression using K-map

→ Implementation of simplified POS expressions using NAND gate

Soln: Truth Table

	I/p				O/p
	A	B	C	D	
0 → January	0	0	0	0	1
1 → February	0	0	0	1	0
2 → March	0	0	1	0	1
3 → April	0	0	1	1	0
4 → May	0	1	0	0	1
5 → June	0	1	0	1	0
6 → July	0	1	1	0	1
7 → August	0	1	1	1	1
8 → September	1	0	0	0	0
9 → October	1	0	0	1	1
10 → November	1	0	1	0	0
11 → December	1	0	1	1	1
12 →	1	1	0	0	X
13 →	1	1	0	1	X
14 →	1	1	1	0	X
15 →	1	1	1	1	X

AB \ CD	00	01	11	10
00	1	1	X	
01				
11				
10				

SOP expression

$f(a, b, c, d)$

\leq

Simplified SOP

$y =$

POS expression

K-map

AB \ CD	00	01	11	10
00	1			1
01	1		1	1
11	X	X	X	X
10		1	1	

SOP expression $\sum m$

$$f(a, b, c, d) = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}B\bar{C}\bar{D} + A\bar{B}\bar{C}\bar{D} + A\bar{B}C\bar{D} + A\bar{B}\bar{C}D + \bar{A}B\bar{C}D + A\bar{B}CD + A\bar{B}C\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D} + A\bar{B}C\bar{D}$$

$$= m_0 + m_4 + d_{12} + d_{13} + m_9 + m_7 + d_{15} + m_{11} + m_2 + m_6 + d_{14}$$

$$= m_0 + m_2 + m_4 + m_7 + m_6 + m_9 + m_{11} + d_{12} + d_{13} + d_{14} + d_{15}$$

$$\sum m = m_0 + m_2 + m_4 + m_6 + m_7 + m_9 + m_{11} + d_{12} + d_{13} + d_{14} + d_{15}$$

Simplified SOP expression using K-map

$$Y = \sum m(0, 2, 4, 6, 7, 9, 11) + d(12, 13, 14, 15)$$

POS expression $\prod M$

$$\prod M = M_0 + M_2 + M_4 + M_6 + M_7 + M_9 + M_{11} + d_{12} + d_{13} + d_{14} + d_{15}$$

Simplified POS expression using K-map

$$Y = \Pi M(0, 2, 4, 6, 7, 9, 11)$$

$$D(12, 13, 14, 15)$$


basic gate implementation using ^{simplified} SOP expression

4> Using 4-
given 8y

Soln:

4> Using 4-variable K-map simplify the Boolean functions
 given by $F(w, x, y, z) = \sum m(1, 3, 4, 6, 8, 9, 11, 13, 15) + \sum d(0, 2, 14)$


Soln:

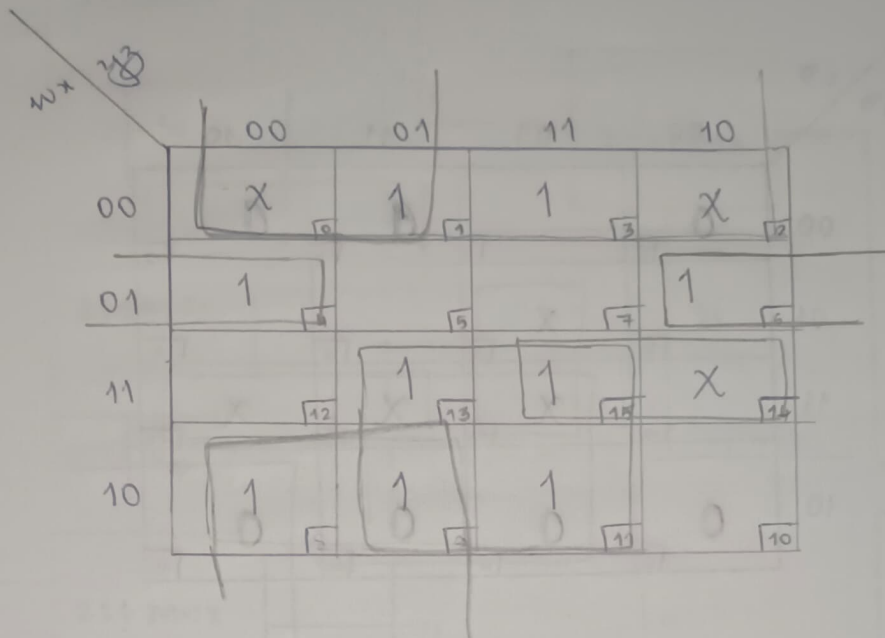

5> Using K-map simplify the product-of-sum from the function given by

$$F(A, B, C, D) = \prod M(0, 2, 3, 8, 9, 10, 11) \cdot \text{don't care } (5, 13, 14, 15)$$

Soln:

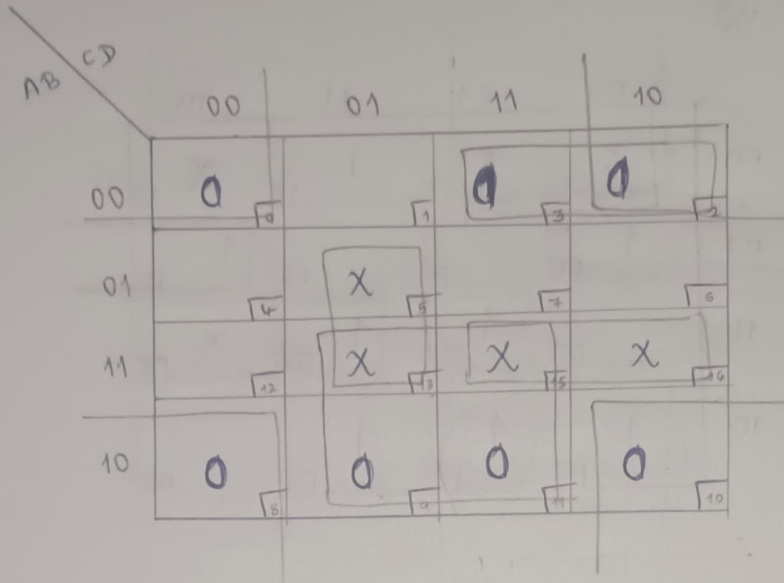

6> Construct

Soln:

I_0 _____ 2
 I_1 _____

I_2 _____ 2
 I_3 _____


I_4 _____ 2
 I_5 _____

I_6 _____ 2
 I_7 _____

slag
 No of

6) Construct 8:1 mux using only 2:1 mux

Soln:

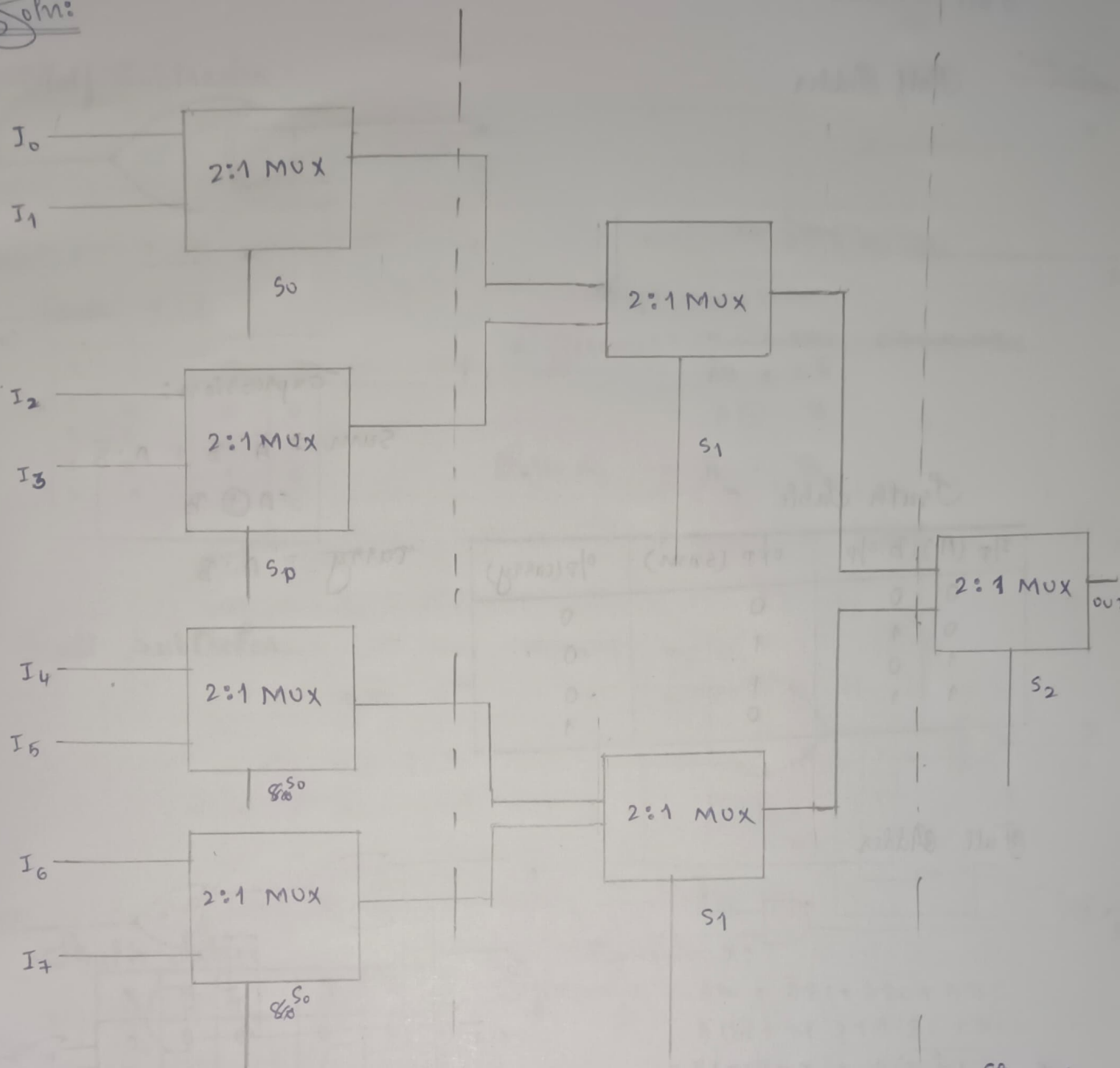


Stage 1
 $\underline{\text{No of MUX}} = 8/2 = 4$

Stage 2
 $\underline{\text{No of MUX}} = 4/2 = 2$

Stage 3
 $\underline{\text{No of MUX}} = 2/2 = 1$

7) Design and explain working Full Adder / Half Adder and Full Subtractor

Soln: Half Adder

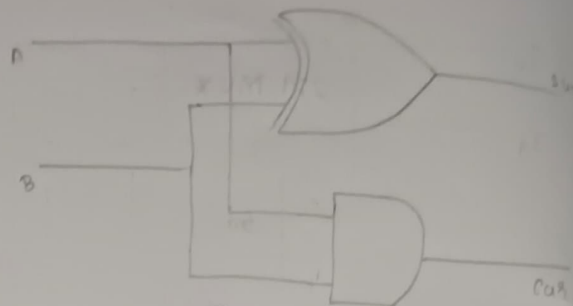

Expression:


$$\text{Sum} = \bar{A} \cdot B + A \cdot \bar{B} \\ = A \oplus B$$

$$\text{Carry} = A \cdot B$$

Truth Table

I/P (A)	(B) O/P	O/P (Sum)	O/P (Carry)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Full Adder

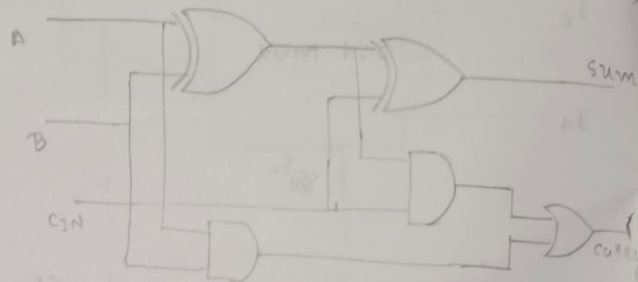

Expression:

$$\begin{aligned} \text{Sum} &= \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + AB C \\ &= \bar{A}(\bar{B}C + B\bar{C}) + A(\bar{B}\bar{C} + BC) \\ &= \bar{A}(B \oplus C) + A(\overline{B \oplus C}) \\ &= \bar{A}(x) + A(\bar{x}) \\ &= A \oplus x \\ &= A \oplus B \oplus C \end{aligned}$$

Let $B \oplus C = x$

Truth Table

A	B	C _{IN}	Sum	CARRY
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\begin{aligned} \text{Carry} &= \bar{A}B \\ &= C \\ &= C \end{aligned}$$

Half Subtractor

Truth Table

X	Y	
0	0	0
0	1	1
1	0	1
1	1	0


Full Subtractor

Truth Table

X	Y	
0	0	0
0	0	0
0	1	1
0	1	0
1	0	0
1	0	1
1	1	1
1	1	0

$$\begin{aligned}\text{Carry} &= \bar{A}Bc + A\bar{B}c + AB\bar{c} + ABC \\ &= c(\bar{A}B + A\bar{B} + AB(\bar{c} + c)) \\ &= c(A \oplus B) + AB\end{aligned}$$

Half Subtractor

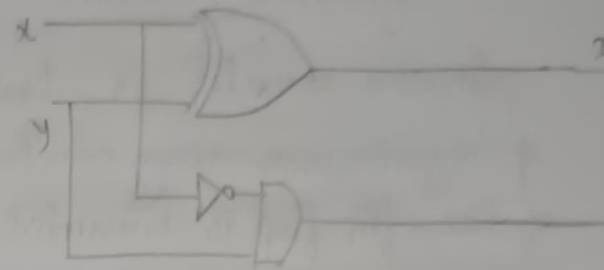

Expression:


$$\begin{aligned}\text{Difference} &= \bar{A}Bc + A\bar{B}c + AB\bar{c} + ABC \\ &= \bar{A}B + A\bar{B} \\ &= A \oplus B\end{aligned}$$

$$\text{Borrow} = \bar{A} \cdot B$$

Truth Table

X	Y	D	B
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Full Subtractor

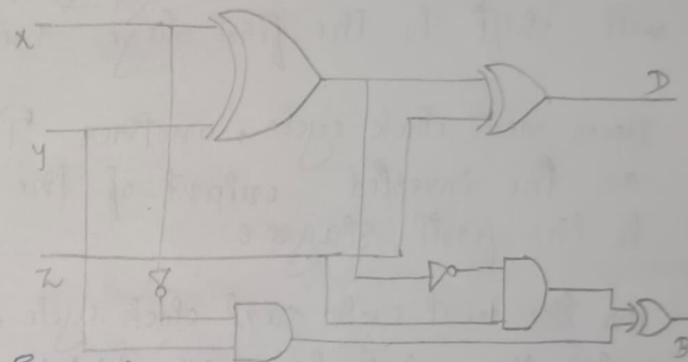

Expression:


$$\begin{aligned}\text{Difference} &= \bar{A}\bar{B}c + \bar{A}B\bar{c} + A\bar{B}\bar{c} + ABC \\ &= \bar{A}(\bar{B}c + B\bar{c}) + A(\bar{B}\bar{c} + Bc) \\ &= \bar{A}(B \oplus c) + A(\bar{B} \oplus \bar{c}) \\ &= \bar{A}(X) + A(\bar{X}) \\ &= A \oplus X \\ &= A \oplus B \oplus c\end{aligned}$$

$$\text{Let } X = B \oplus c$$

$$\begin{aligned}\text{Borrow} &= \bar{A}\bar{B}c + \bar{A}B\bar{c} + A\bar{B}\bar{c} + ABC \\ &= \bar{A}\bar{B}c + ABC + \bar{A}B\bar{c} + \bar{A}Bc \\ &= c(\bar{A}\bar{B} + AB) + \bar{A}B(\bar{c} + c) \\ &= c(\bar{A} \oplus B) + \bar{A}B \\ &= \bar{A}B + c(\bar{A} \oplus B)\end{aligned}$$

Truth Table

X	Y	Z	D	B
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

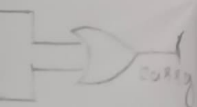

$$\text{Let } B \oplus c = X$$

8> Describe the working of Johnson Counter along with timing table and shift table

Soln:

Johnson Counter

Johnson counter or Twisted ring counter is type of synchronous ring counter in which the complemented output of the flip flop is connected with the input of the first flip flop. The Johnson counter can be made with D flips or JK flip flops in the cascade setup.

Working

The default state of Johnson counter is 0000 thus before starting the clock input we need to clear the counter using clear input.

Whenever the clock edge hits the counter the output of each flip flop will transfer to the next stage (flip flop) but the inverted flip flop will shift to the first stage making the state 1000.


Upon next clock cycle, another '1' will stack in from the left side as the inverted output of the last stage will be shifted to the first stage.

On the next cycle next clock cycle, another '1' will add from left until the state becomes 1111.

Now the last flip flop's output is '1', the next clock cycle will shift the invert of the last flip flop which is '0' into the first flip flop. It will result in stacking '0' from the left side. This stacking of the first 0 will make the state 1111 into 0111.

The next coming clock cycles will stack in 0's from the left making the states 0011, 0001 and 0000 with each clock cycle. Eventually it reaches its default state and it starts from the beginning again.

Timing diagram

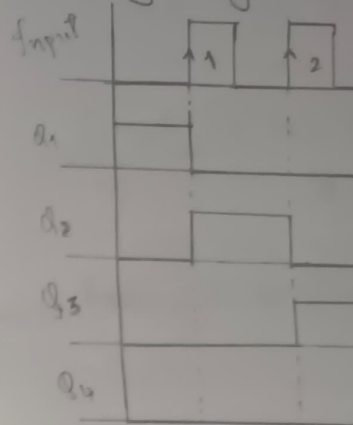

Shift table

CP	Q ₄
0	0
1	1
2	1
3	1
4	1
5	0
6	0
7	0
8	0

a) The 3-bit in is '000', '001' having letters '0' input condition determine the

→ Truth table

→ SOP expression


→ POS expression

→ Simplified S

→ Basic gate

→ Simplified

Timing diagram

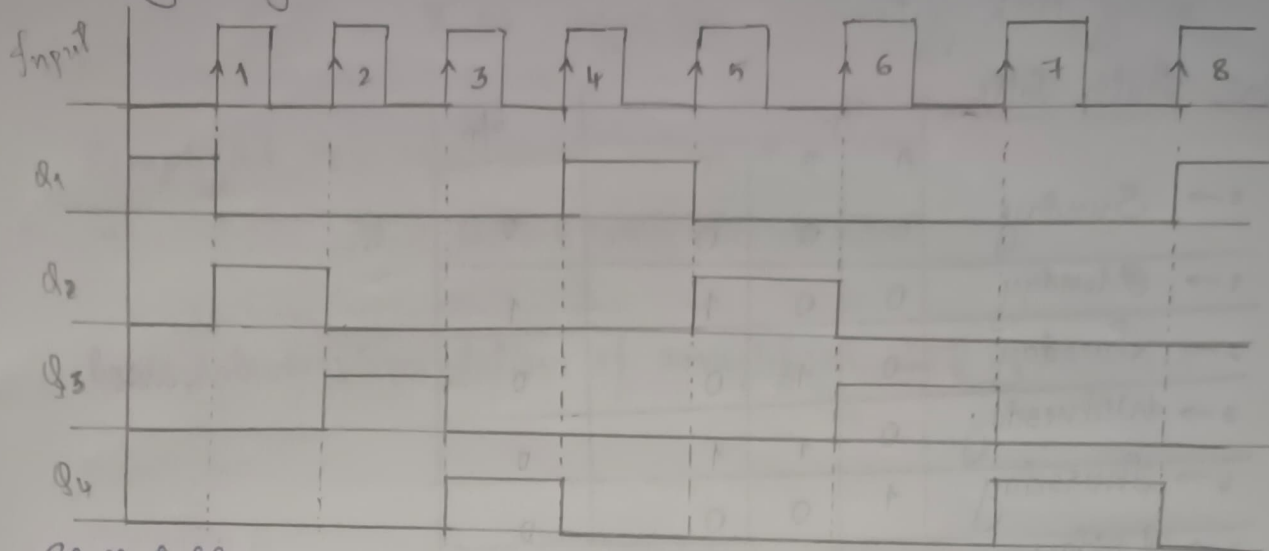

Shift table

CP	Q_1	Q_2	Q_3	Q_4
0	0	0	0	0
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1
5	0	1	1	1
6	0	0	1	1
7	0	0	0	1
8	0	0	0	0

CP \rightarrow clock pulse

a) The 3-bit inputs for the days of the week starting from Sunday is '000', '001' and so on, and the output for the days having letters 'E' and/or 'u' is '0' else a '1'. Treat the input condition '111' as don't care. For the above specifications determine the following

\rightarrow Truth Table

\rightarrow SOP expression Σm

\rightarrow POS expression ΠM

\rightarrow Simplified SOP expression using K-map

\rightarrow Basic gate implementation of simplified SOP expression

\rightarrow Simplified POS expression using K-map

→ Implementation of simplified POS expressions using NOR gates

POS ex

Soln: Truth Table

	I/P			O/P
	A	B	C	
0 → Sunday	0	0	0	0
1 → Monday	0	0	1	1
2 → Tuesday	0	1	0	0
3 → Wednesday	0	1	1	0
4 → Thursday	1	0	0	0
5 → Friday	1	0	1	1
6 → Saturday	1	1	0	0
7 →	1	1	1	X

Simplified

basic gate

ab \ cd				
	00	01	11	10
00	0	1	0	0
01	0	1	X	0
11	0	0	0	0
10	0	0	0	0

SOP expression $\sum m$

$$f(A, B, C) = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}C$$

$$= m_1 + m_5 + d_7$$

$$\sum m = m_1 + m_5 + d_7$$

SOP

Simplified expression using K-map

$$Y = \sum m(1, 5) + d(7)$$

POS expression πM

$$\pi M = M_1 + M_5 + D_7$$

Simplified POS expression using K-map

$$Y = \pi M(1, 5) \cdot D(7)$$

Basic gate implementation of simplified SOP expression

x	y	z	w
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

x	y	z
0	0	0
1	1	0
1	0	1
0	1	1

10) Illustrate T, JK flip flop with the help of logic diagram and the characteristic table


~~Soln:~~ T flip flop

The T flip flop means Toggle flip flop. It changes the output on each clock edge and gives an output that is half the frequency of the signal to the input.

The most common flip flop used to make the T flip flop is MC74HC73A (Dual JK flip flop).

The T flip flop can be derived from JK, SR, and D flip flop. The easiest way to construct T flip flop is from JK flip flop.

Logic diagram

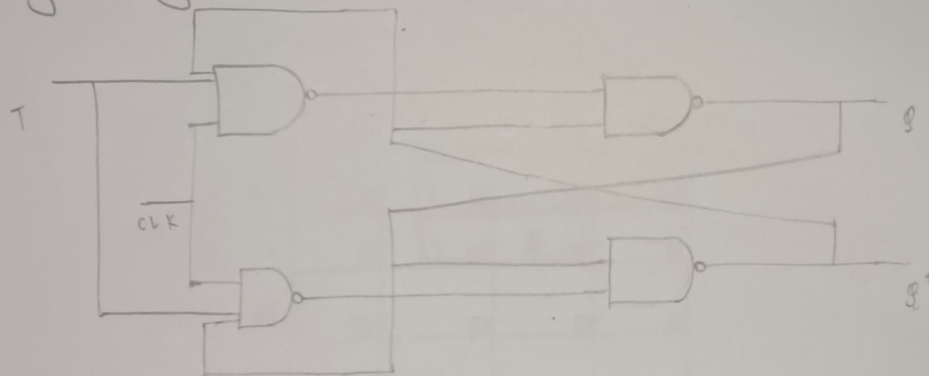

Truth Table

T	Q_N	Q_{N+1}
0	0	0
0	1	1
1	0	1
1	1	0

characteristic equation for T flip flop


$$Q_{N+1} = Q_N T + Q_N T^1 = Q_N \text{ XOR } T$$

JK flip flop

The JK flip flop is no change

The JK flip flop it is consid

Logic diagram

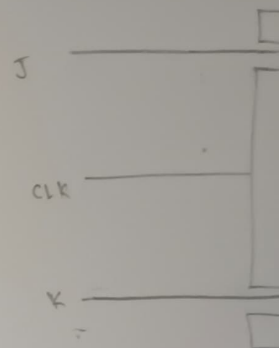

Truth Table


J	K	
0	0	
0	0	
0	1	
0	1	
1	0	
1	0	
1	1	
1	1	

JK flip flop

The JK flip flop is similar to the SR flip flop but there is no change in state when the J and K inputs are low.

The JK flip flop is the most widely used flip flop and it is considered to be the universal flip flop circuit.

Logic diagram

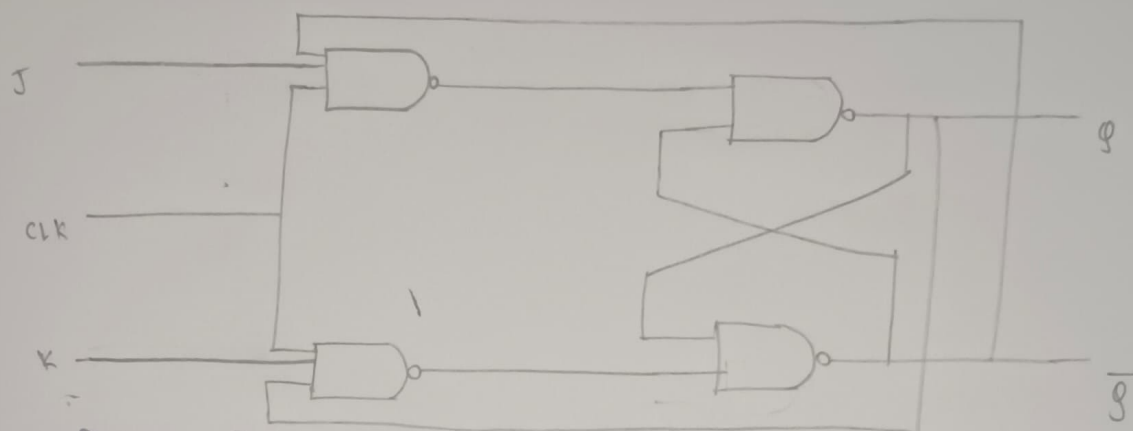

Truth Table

J	K	Q_N	Q_{N+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Characteristic equation for JK flip flop

$$Q_{N+1} = JQ_N' + K'Q_N$$